
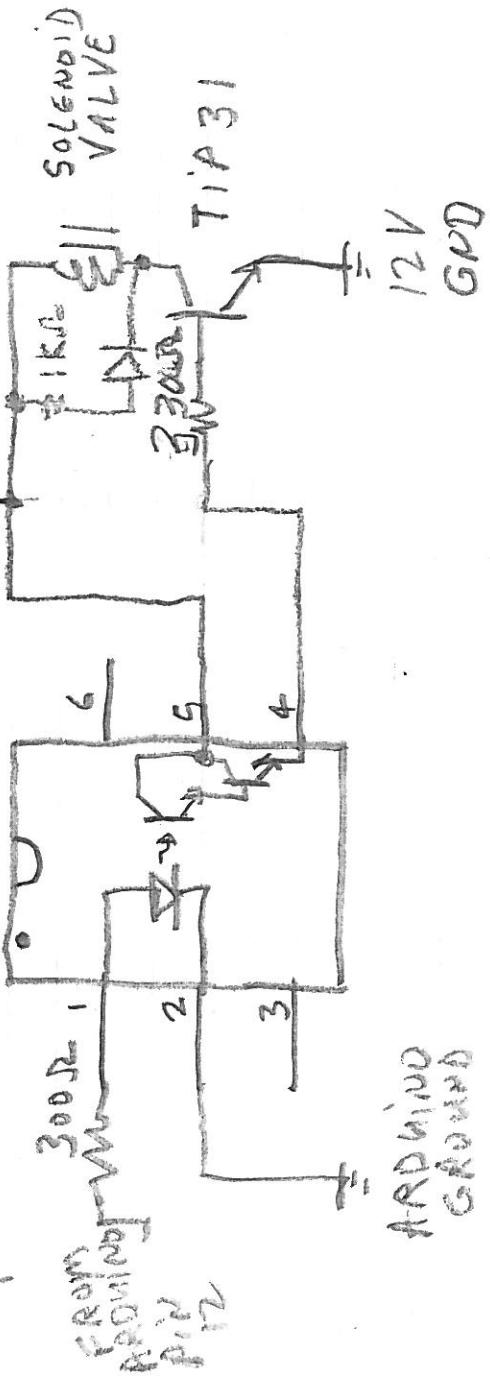


SOLENOID VALVE CIRCUIT

USE
BLINK 7 SEC.
PROGRAM
4N32

POWER SUPPLY
12VDC = 4VDC

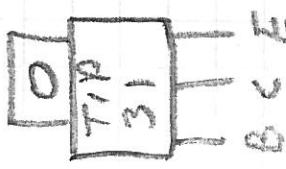

ARDUINO PNEUMATIC
PROJECT
EMT 2320
PROOF OF MOTION
12/2/14
Rev I 12/9/14
e2ea

NOTE: TEAM REPORT
WAIT A FEW DAYS GIVE A POWER POINT
PRESENTATION (EVERYONE SPEAK)
DO INTERNET RESEARCH